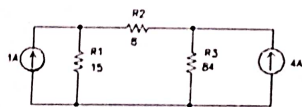


Node and Mesh analysis Numerical

Problems for Mesh & Nodal Analysis

#1.

Figure 1 - Problem 1
Find the voltage across R2.



Answer: Answer: VR2 = 24v with right side more positive

Nodal Equations

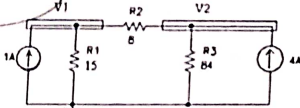


Figure 1 - Problem 1

Node 1 $-1A + V1/15 + (V1 - V2)/8 = 0$

Node 2 $(V2 - V1)/8 + V2/8 - 4A = 0$

Answer: VR2 = 24v (right more +)

Mesh Equations

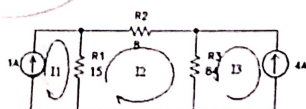


Figure 1 - Problem 1

Loop 1 $I1 = 1A$

Loop 2 $15(I2 - I1) + 8I2 + 84(I2 + I3) = 0$

Loop 3 $I3 = -4A$

Answer: VR2 = 24v (right more +)

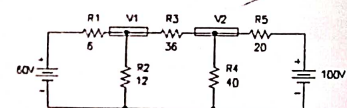


Figure 2 - Problem 2

Find the node voltages V1 and V2.

1.

Nodal Equations

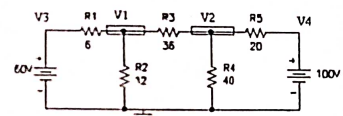


Figure 2 - Problem 2

Node 1 $(V1 - V3)/6 + V1/12 + (V1 - V2)/36 = 0$

Node 2 $(V2 - V1)/36 + V2/40 + (V2 - V3)/20 = 0$

Node 3 $V3 = 60$

Node 4 $V4 = 100$


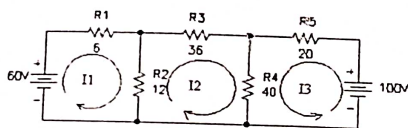



Figure 2 - Problem 2

Loop 1 $-60v + 6 \cdot I1 + 12 \cdot (I1 - I2) = 0$
 Loop 2 $12 \cdot (I2 - I1) + 36 \cdot I2 + 40 \cdot (I2 + I3) = 0$
 Loop 3 $-100v + 20 \cdot I3 + 40 \cdot (I3 + I2) = 0$
 Answer: $V1 = 42v$, $V2 = 60v$

3. Find the current through R2 and R3

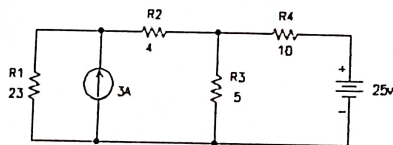

Nodal equations:

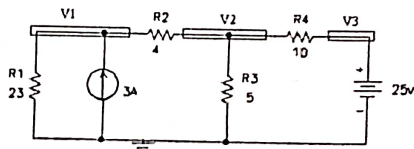


Node 2: $(V2 - V1)/4 + V2/5 + (V2 - V3)/10 = 0$

Node 3: $V3 = 25v$

Answer: $IR2 = (V1 - V2)/4 = 2A$, $IR3 = V2/5 = 3A$

Mesh equation

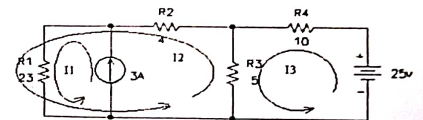


Loop 1 $I1 = 3A$

Loop 2 $5 \cdot (I2 - I3) + 4 \cdot I2 + 23 \cdot (I2 + I1) = 0$

Loop 3 $-25v + 10 \cdot I3 + 5 \cdot (I3 - I2) = 0$

Answer: $IR2 = (V1 - V2)/4 = 2A$, $IR3 = V2/5 = 3A$

4. Find the voltage across R3

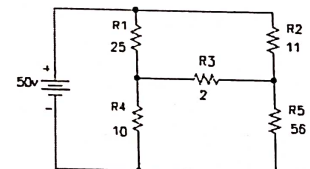

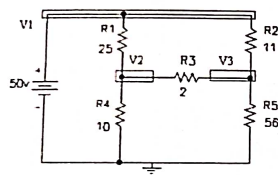


Figure 4 - Problem 4

Node 1 $V1 = 50v$
 Node 2 $(V2 - V1)/25 + V2/10 + (V2 - V3)/2 = 0$
 Node 3 $(V3 - V1)/11 + V3/56 + (V3 - V2)/2 = 0$

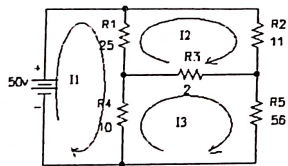


Figure 4 - Problem 4

Loop 1 $-50v + 25(I1 - I2) + 10(I1 - I3) = 0$
 Loop 2 $25(I2 - I1) + 11I2 + 2(I2 - I3) = 0$
 Loop 3 $10(I3 - I1) + 2(I3 - I2) + 56I3 = 0$
 Answer: $VR3 = V3 - V2 = 3v$

5. Find the current through R3.

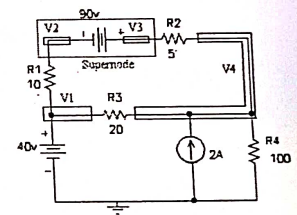
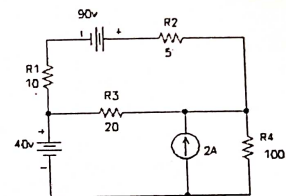


Figure 5 - Problem 5

Node 1 $V1 = 40v$
 Supernode 1 $V2 + 90 = V3$
 Supernode 2 $(V2 - V1)/10 + (V3 - V4)/5 = 0$
 Node 4 $(V4 - V3)/5 + V4/100 - 2A + (V4 - V1)/20 = 0$
 Answer: $IR3 = (V4 - V1)/R3 = 3A$

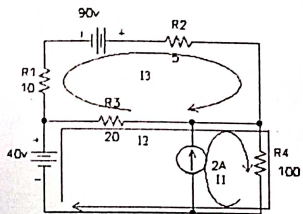


Figure 5 - Problem 5

Loop 1 $I_1 = 2A$
 Loop 2 $-40V - 20(I_2 - I_3) + 100(I_2 + I_1) = 0$
 Loop 3 $10I_1 - 90V + 5I_3 + 20(I_3 - I_2) = 0$
 Answer: $IR_3 = (V_4 - V_1)/R_3 = 3A$

6. Find the voltage across the 1A current source

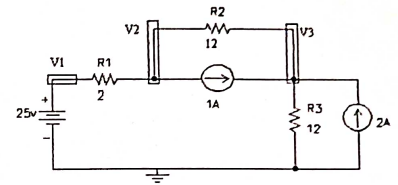
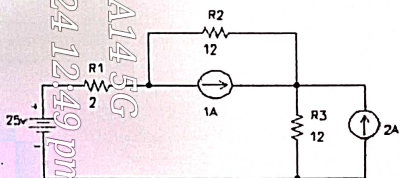


Figure 6 - Problem 6

Node 1 $V_1 = 25V$
 Node 2 $(V_2 - V_1)/2 + (V_2 - V_3)/12 + 1A = 0$
 Node 3 $(V_3 - V_2)/12 - 1A + V_3/12 - 2A = 0$
 Answer: $V(1A \text{ source}) = V_3 - V_2 = 6V$

Mesh analysis


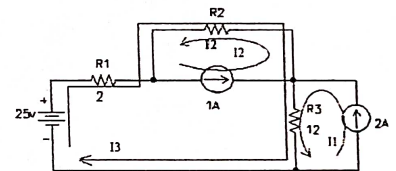


Figure 6 - Problem 6

Loop 1 $I_1 = 2A$
 Loop 2 $I_2 = 1A$
 Loop 3 $-25V + 2I_3 + 12(I_3 - I_2) + 12(I_3 + I_1) = 0$
 Answer: $V(1A \text{ source}) = VR_2 = 12(I_2 - I_3) = 6V$
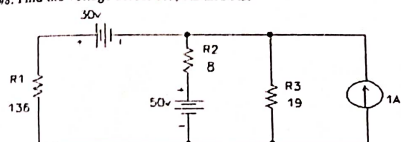
#8. Find the voltage across R1, R2 and R3.



Nodal analysis:


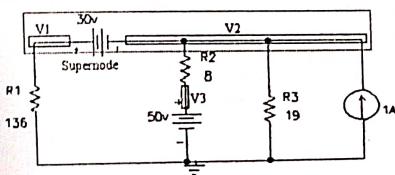


Figure 8 - Problem 8


Answer: $V_{R1} = 68\text{V}$; $V_{R2} = 12\text{V}$; $V_{R3} = 38\text{V}$

Node 1: $V_1 - 30 = V_2$
 Supernode: $V_1/136 + (V_2 - V_3)/8 + V_2/19 - 1\text{A} = 0$
 Node 3: $V_3 = 50\text{V}$

Mesh analysis:

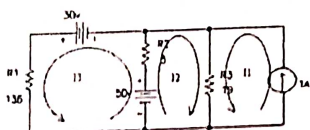

#9. Find the current labeled "I".

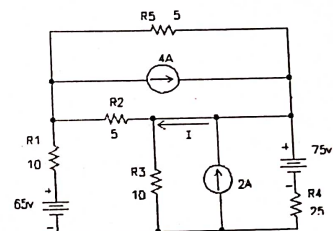

Nodal analysis:

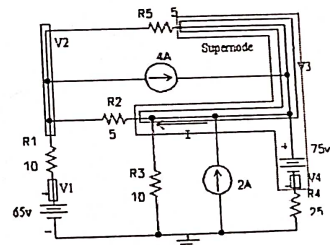


Figure 9 - Problem 9

Node 1: $V_1 = 65\text{V}$
 Node 2: $(V_2 - V_1)/10 + (V_2 - V_3)/5 + 4\text{A} = 0$
 Node 4: $V_4 + 75 = V_3$

Mesh analysis:

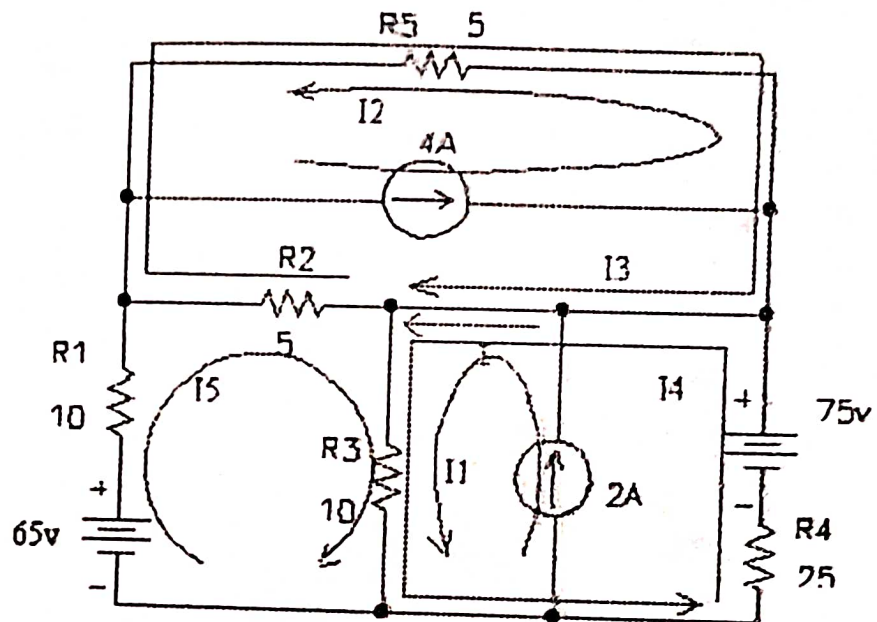


Figure 9 - Problem 9

Loop 1

$$I_1 = 2A$$

Loop 2

$$I_2 = 4A$$

Loop 3

$$5(I_3 - I_5) + 5(I_3 - I_2) = 0$$

Loop 4

$$25I_4 - 75v + 10(I_4 + I_1 + I_5) = 0$$

Loop 5

$$-65v + 10I_5 + 5(I_5 - I_3) + 10(I_5 + I_1 + I_4) = 0$$

$$\text{Answer: } I = I_1 + I_4 - I_3 = 6A$$

Numerical based on kvl or kcl

Kirchhoff's Voltage law: The algebraic sum of all the voltages in any mesh (closed circuit) is zero.

Determination of signs while solving problems-

1. **Voltage Source:** A positive sign is assigned to the EMF when going from the negative terminal of the voltage source to the positive terminal since there is an increase in potential. On the other hand, when moving from the positive terminal to the negative terminal, potential drops and the EMF is marked as negative.



eeGATE

2. **Resistance:** The potential drop is negative when passing through the resistance in the same direction as the current flow because the potential decreases. However, if the resistance is traversed in the opposite direction to the current flow, the potential increases, resulting in a positive voltage drop.



eeGATE

Note:

1. Consider the second polarity of the voltage source / battery and resistance in the direction of current while solving the problems.
2. To simplify calculations, it is advisable to always assume that the current is flowing clockwise.

Find the power consumed by the combination of resistances when connected to a voltage source of 100 V at terminals P-Q (Fig. 1.9).

(Ans: 3.125 kW)

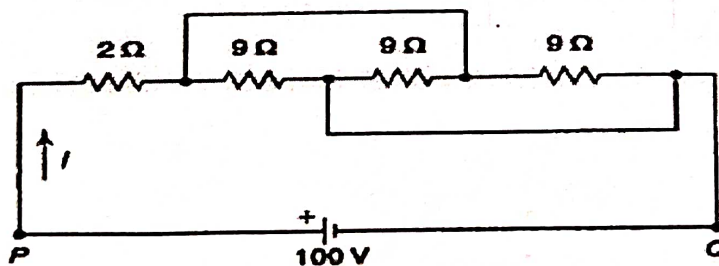


Fig. 1.9

[Hint: Fig. 1.9 can be reduced as shown below:


Galaxy A14 5G

30 April 2024 12:50 pm

Numerical based on kvl or kcl



02

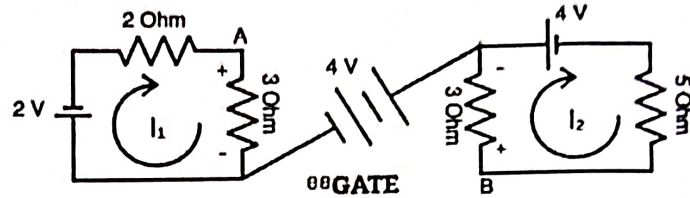Find potential difference between X and Y.




03

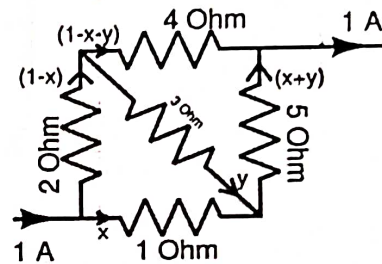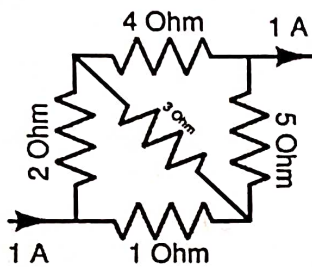Find current flowing through all resistors.




04

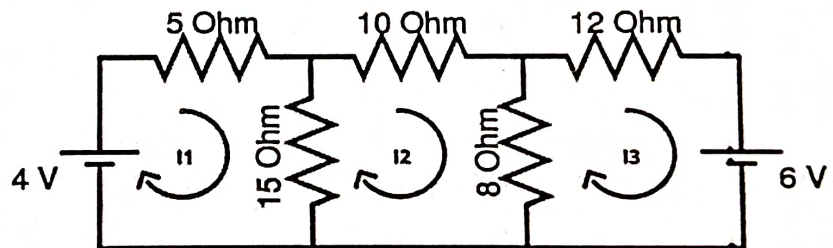By using KVL find Current flowing through 10 Ω resistance.



05

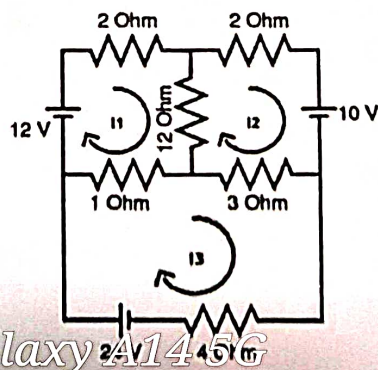
By using Kirchhoff's voltage law (KVL) / Mesh analysis find the current flowing through a 4 Ω resistor.




Galaxy A1456
30 April 2024 12:50 pm

Numerical based on kvl or kcl

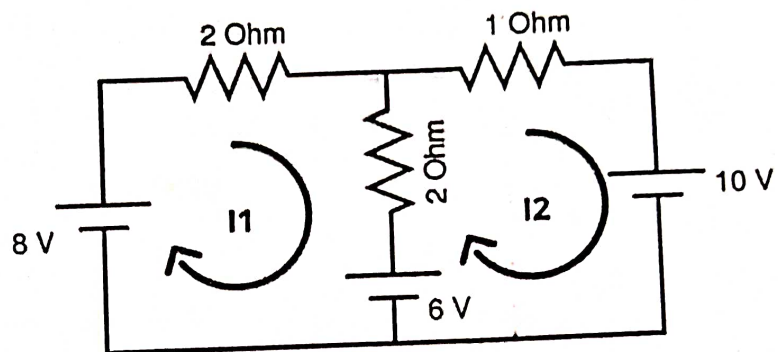
06
By using Kirchhoff's voltage law (KVL) / Mesh analysis find the current flowing through a $1\ \Omega$ resistor.



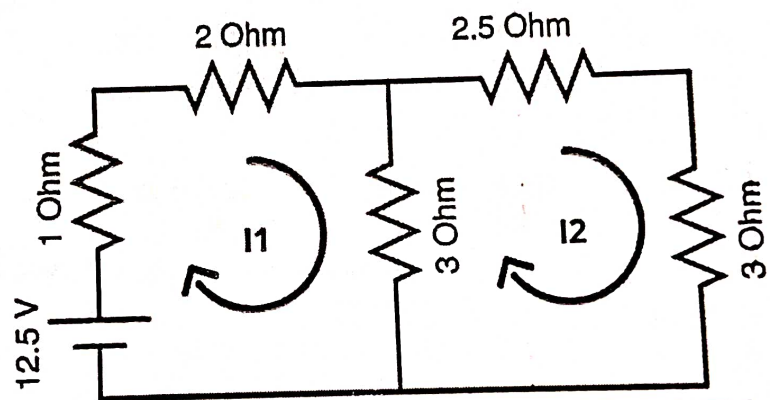07
By using Kirchhoff's voltage law (KVL) / Mesh analysis find the current flowing through all resistances.



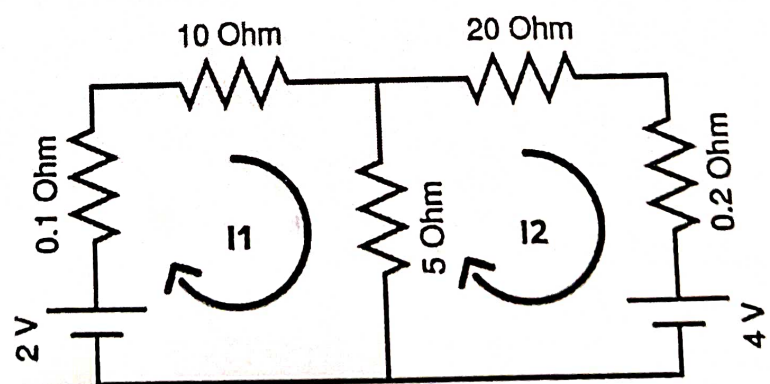08
By using Kirchhoff's voltage law (KVL) / Mesh analysis find the current flowing through a $5\ \Omega$ resistor.




Galaxy A14 5G


30 April 2024 12:50 pm

Numerical based on kvl or kcl

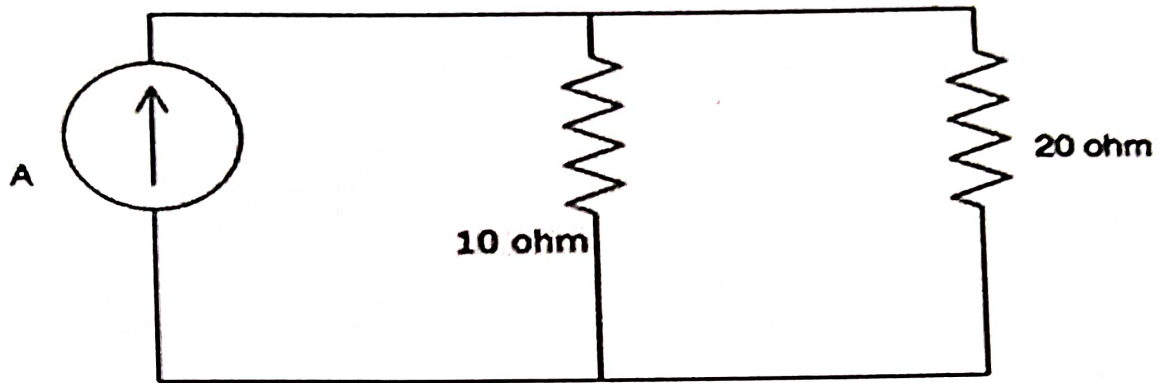Q2 Calculate the current across the 20 ohm resistor.




Q10 Calculate the current A.

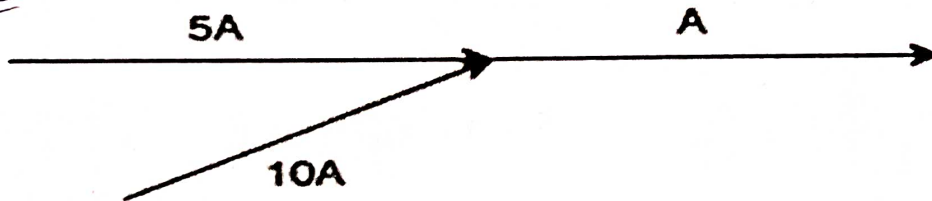

CA

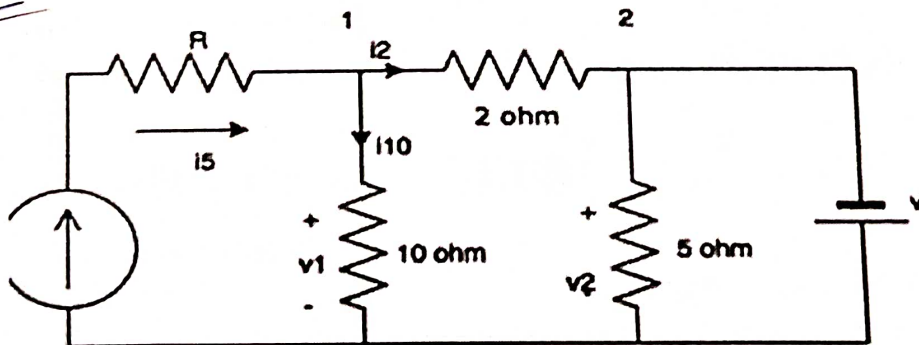Q11 Find the value of v if $v_1 = 20V$ and value of current source is 6A.



Galaxy A14 5G

30 April 2024 12:51 pm

Numerical based on kvl or kcl

Q12

Find the equivalent resistance between points a and b of the infinite ladder shown in Fig. 1.13.

(Ans: $R_{eq(a-b)} = \frac{1+\sqrt{5}}{2} \cdot R$)

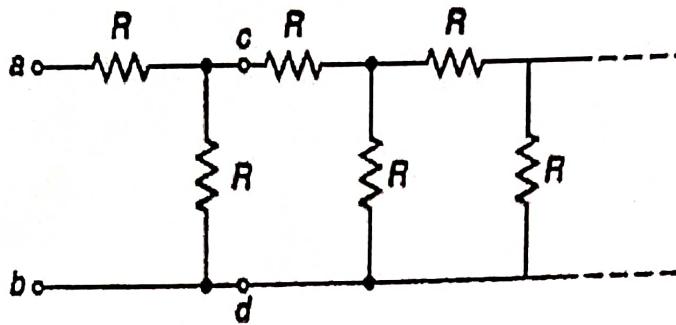


Fig. 1.13

Q13

KCL is applied at _____

Loop

Node


Both loop and node

Neither loop nor node

[View Answer](#)

Q14

What is the value of the current I ?

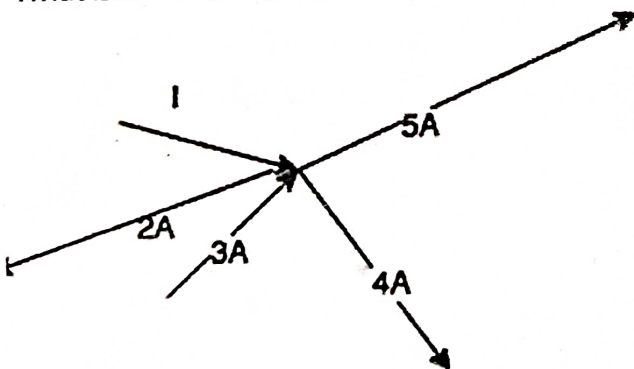


$$I + 3 = 5A + 4A$$

Numerical based on kvl or kcl

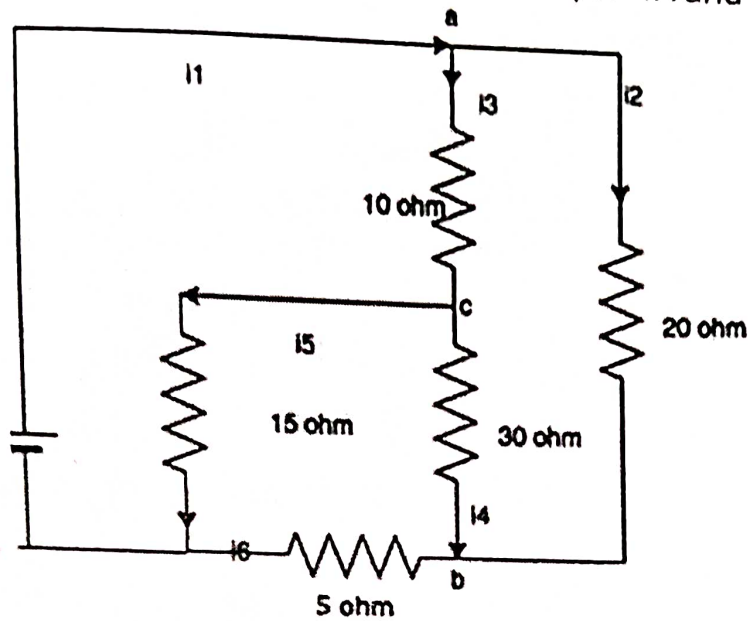
Q15

Find the value of i_2 , i_4 and i_5 if $i_1=3A$, $i_3=1A$ and $i_6=1A$.




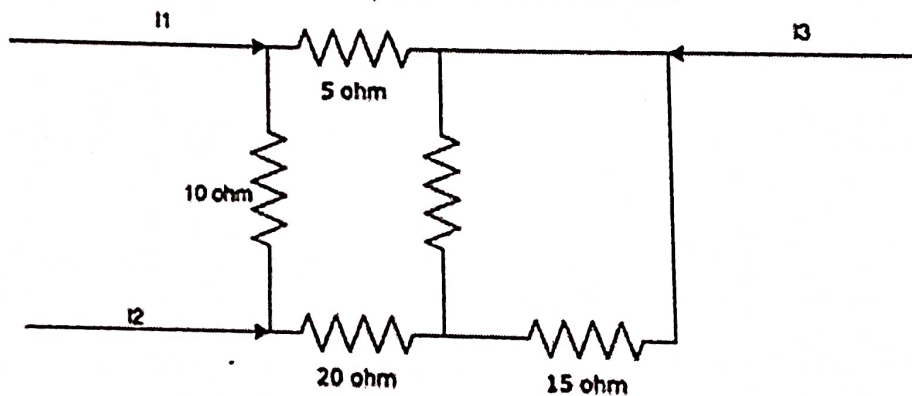Q16

Calculate the value of i_3 , if $i_1=2A$ and $i_2=3A$.



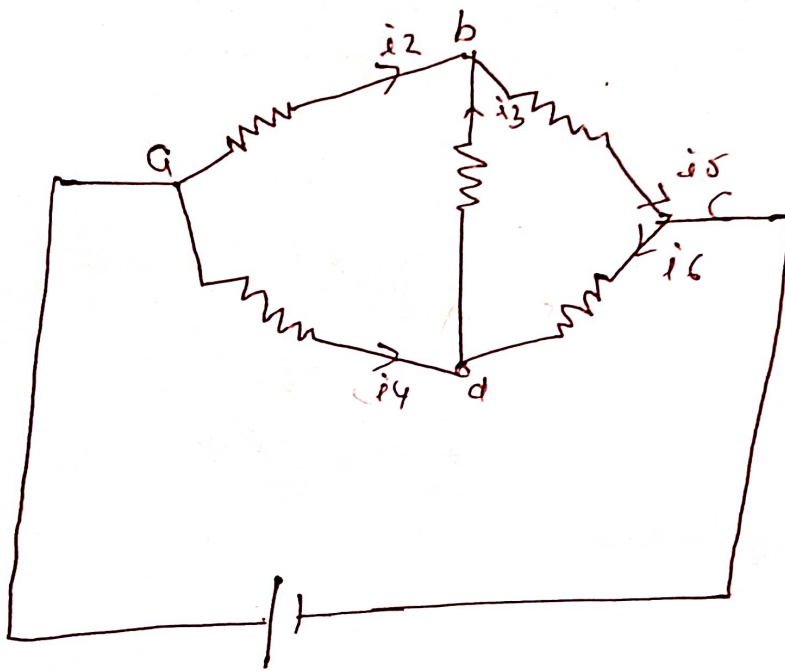Q19 find the current unknowns i_4, i_3, i_6 given
 $i_1 = 20A$ $i_2 = 12A$ $i_5 = 8A$



Q20

